

EE5811 - FPGA Lab Assignment 1

EE19MTECH11032 - Bala Priya C

Download the LaTeX code from:

<https://github.com/balapriyac/EE5811-FPGA-lab/tree/main/Assignment-1>

1 QUESTION

[CBSE 2013 Q6 (b)] Obtain the Boolean expression for the logic circuit shown below:

 


Fig. 1: Logic circuit

2 SOLUTION

The algebraically simplified Boolean expression for F is shown below.

$$F = (X' + Y) + YZ' \quad (2.1)$$

$$= X' + (Y + YZ') \quad (2.2)$$

$$= X' + Y(1 + Z') \quad (2.3)$$

$$= X' + Y(1 + Z') \quad (2.4)$$

$$= X' + Y \text{ since } 1 + Z' = 1 \quad (2.5)$$

$$\Rightarrow F = X' + Y \quad (2.6)$$

3 TRUTH TABLE

The truth table corresponding to F for various choices of input X, Y, Z is shown below:

X	Y	Z	F
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

4 SIMPLIFICATION USING KARNAUGH MAP

YZ \ X	00	01	11	10
0	1	1	1	1
1	0	0	1	1

Fig. 2: K-Map for $F = X' + Y$

5 IMPLEMENTATION USING NAND LOGIC

$$F = X' + Y \quad (5.1)$$

$$= (X.Y')' \quad (5.2)$$

$$\text{since } (A.B)' = A' + B' \quad (5.3)$$

$$\Rightarrow F = (X.Y')' \text{ (using NAND logic)} \quad (5.4)$$

 


Fig. 3: Logic circuit using NAND logic